

## DEMUX

DEMUX or De-multiplexer is a data distribution combinational circuit. It works in a reverse way of the multiplexer. The DEMUX has 1 i/p port &  $2^n$  o/p lines. Here  $n$  signifies the selection line for a DEMUX. As per selection line value, the DEMUX i/p lines will be connected to receive the o/p. Demultiplexer receives digital information from a single source & converts it into several sources.

### Advantages :-

- \* Increases the efficiency of the particular communication system
- \* DEMUX can decode the signal input

